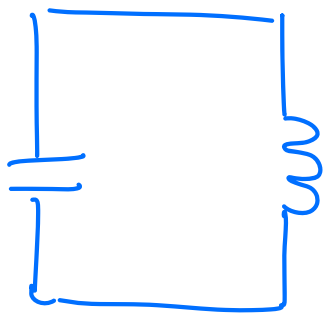


After the switch closes at  $t=0$ ,  
Our circuit will assume 2 states:

State 1: Diode is OFF, so the middle branch has an open.




Initial conditions:

$$V_c @ t(0)_- = t(0)_+ = V_x = 1000V$$

$$I_L = 0A$$

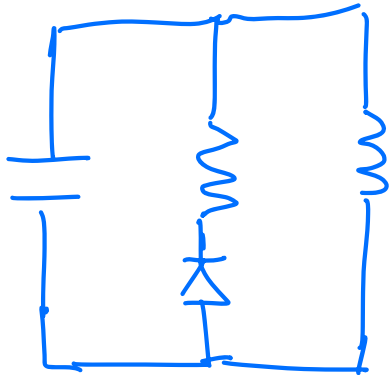State 2: Diode turns on when  $V_x$  hits 0V... RLC circuit,



Initial conditions:

$$V_x = 0V$$

$$I_L = 4045.2A$$

$I_L$  is @ MAX bc C has fully discharged into L...


$$\frac{1}{2} C V_x^2 = \frac{1}{2} L I_m^2$$

$\uparrow \quad \uparrow \quad \quad \uparrow$   
 1804F 1000      114H

$$180 = L I_m^2 \rightarrow 4045.2A$$

Will have a piecewise fn to represent circuit behavior after  $t=0$ .

State 1 diff eq.

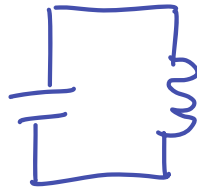

$$I_L(0) = 0 \text{ A}$$

$$V_C(0) = 1000 \text{ V}$$

$$L \frac{di}{dt} + \frac{1}{C} \int i dt = 0$$

$$\hookrightarrow \frac{di^2}{dt^2} L + \frac{1}{C} i(t) = 0$$

$$\hookrightarrow \frac{di^2}{dt^2} + \frac{1}{LC} i(t) = 0$$

$$\hookrightarrow s^2 k e^{st} + \frac{1}{LC} k e^{st} = 0$$

$$\hookrightarrow s^2 + \frac{1}{LC} = 0$$

$$\hookrightarrow i(t) = k_1 e^{j\omega_0 t} + k_2 e^{-j\omega_0 t}$$

$$\hookrightarrow i(t) = A_1 \cos \omega_0 t + A_2 \sin \omega_0 t$$

$$V = L \frac{di}{dt} \rightarrow \frac{V(0)}{L} = \frac{di}{dt}$$

$$\rightarrow i(t) = A_1 \cos \omega_0 t + A_2 \sin \omega_0 t$$

$$i(0) = 0 \text{ A} \quad \begin{matrix} \nearrow \\ 0 \end{matrix} \quad \begin{matrix} \nearrow \\ 0 \end{matrix}$$

$$i(t) = A_1 \rightarrow A_1 = 0$$

$$\rightarrow i(t) = A_2 \sin(\omega_0 t)$$

$$\frac{di}{dt} = \frac{d}{dt} (A_2 \sin(\omega_0 t))$$

$$\rightarrow = A_2 \omega_0 \cos(\omega_0 t) \quad @ t=0$$

$$\frac{di}{dt} = A_2 \omega_0$$


$$\hookrightarrow \frac{V_0}{L} = A_2 \omega_0$$

$$\frac{1000 \text{ V}}{114 \text{ H} \sqrt{\frac{114 \text{ H}}{1804 \text{ F}}}} = A_2 = 4045.2$$

$$\underline{i(t) = 4045.2 \sin(22473 \cdot t)}$$

## State 2 DiffEq:

Initial conditions:

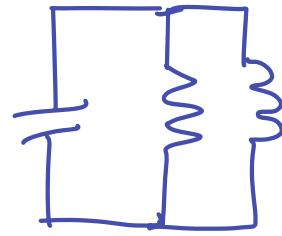

$$V_C(t_x) = 0V$$

$$i_L(t_x) = 4045.2A$$

$$\hookrightarrow s^2 + \frac{s}{RC} + \frac{1}{LC} = 0$$

$$\hookrightarrow i(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

$$\alpha = \frac{1}{2RC} = 32,679$$

$$\alpha > \omega_0$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = 22473$$

$\rightarrow$  overdamped

$$\hookrightarrow \begin{aligned} i(t) &= A_1 e^{s_1 t} + A_2 e^{s_2 t} \\ i'(t) &= A_1 s_1 e^{s_1 t} + A_2 s_2 e^{s_2 t} \end{aligned}$$

$$s_1, s_2 = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

$$s_1 = -8953 \quad s_2 = -56404$$

$$i(t) = A_1 e^{-8953t} + A_2 e^{-56404t}$$

$$i(t_x) = A_1 + A_2 = 4045.2$$

$$\frac{di}{dt} = A_1 s_1 + A_2 s_2$$

$$\frac{di}{dt} = A_1 (-8953) + A_2 (-56404)$$

$$\uparrow \frac{0}{L}$$

$$A_1 + A_2 = 4045.2$$

$$-8953A_1 - 56404A_2 = 0$$

$$A_1 = 4808.4 \quad A_2 = -763.2$$

Equation 2:

$$i(t) = 4808.4 e^{-8953t} - 763.2 e^{-56404t}$$


---

$$1) \quad i(t) = \begin{cases} 0 \leq t \leq t_1 & 4045.2 \sin(22473t) \\ t_1 < t & 4808.4e^{-8953t} - 763.2e^{-56404t} \end{cases}$$

$$2) \quad \frac{1}{2} C V_x^2 = \frac{1}{2} L I_m^2 \quad \underline{I_m = 4045.2 \text{ A}}$$


$\begin{matrix} \uparrow & \uparrow & \uparrow \\ 1804 \text{ F} & 1000 & 114 \text{ H} \end{matrix}$

$$180 = L I_m^2 \rightarrow 4045.2 \text{ A}$$

$$3) \quad 1 = \sin\left(22473 \cdot \underbrace{t}_{\frac{\pi}{2}}\right) \rightarrow t_x = \underline{6.99 \times 10^{-5} \text{ seconds}}$$


$$4) \quad \frac{1}{2} C V_x^2 = \underline{90 \text{ W}}$$

PLECS SIM:

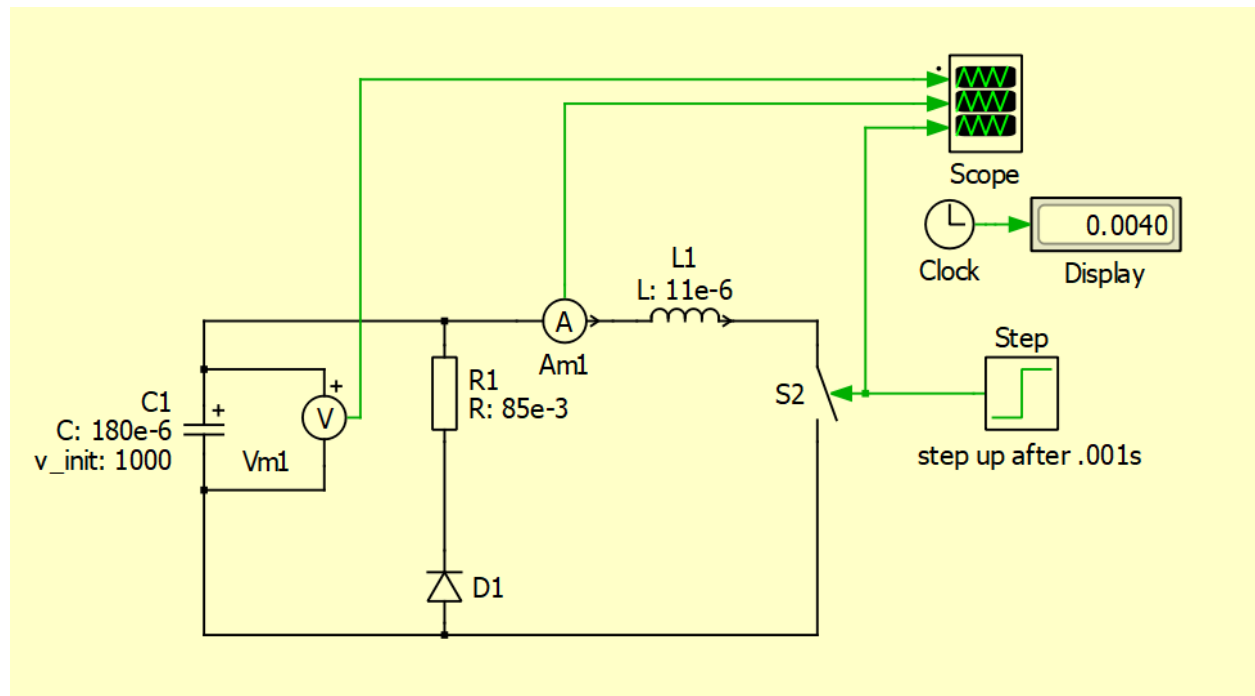




b)  $V_{c\_init} = 1000V$

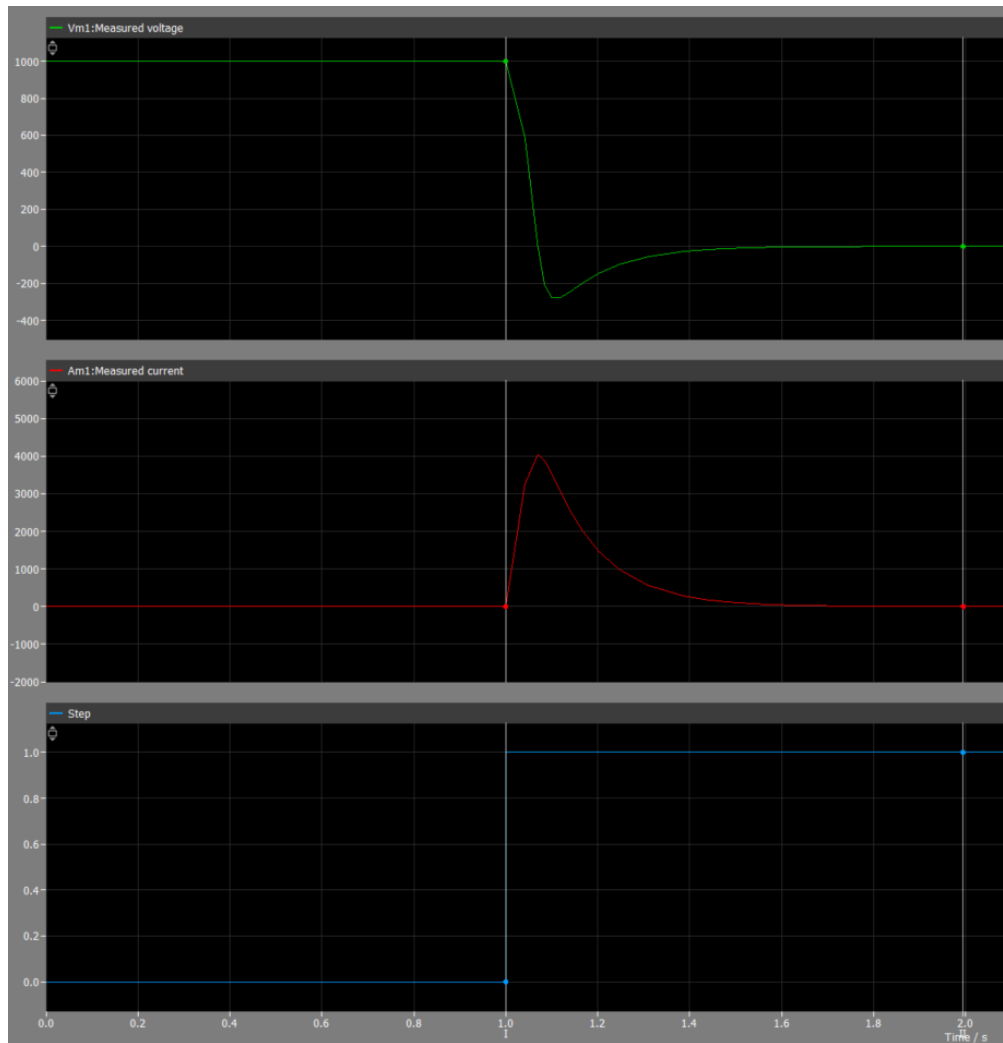

Green: Capacitor Voltage

Red: Inductor Current

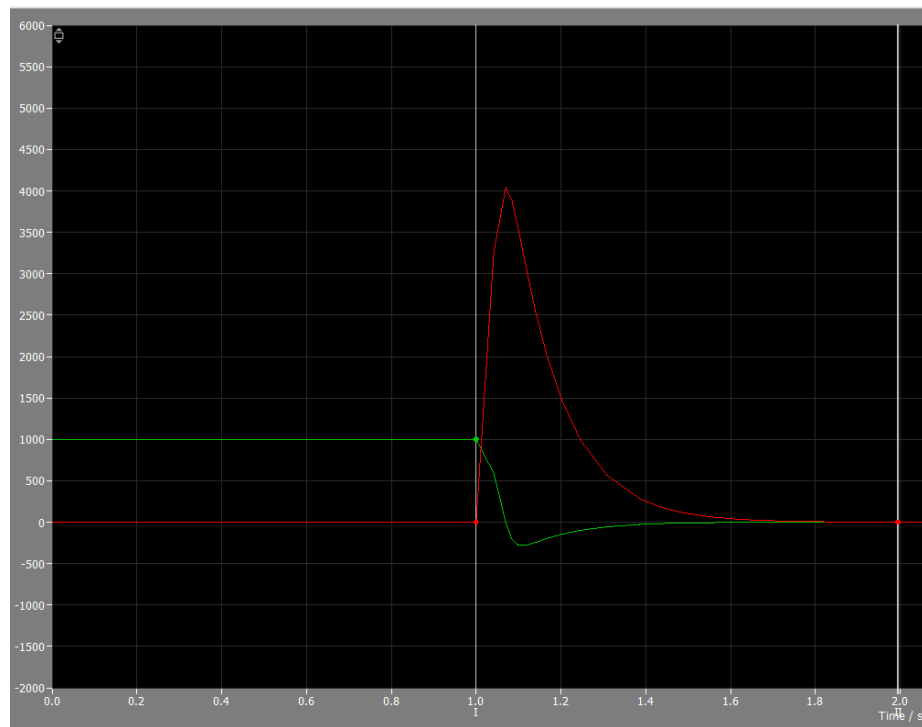Blue: My switch (activated via step function)




$V_C$ ,  $I_L$  plotted together

c)

Less current. In simulating various  $V_{c\_init}$ , I found no change to  $t$

$V_{c\_init} = 500V$

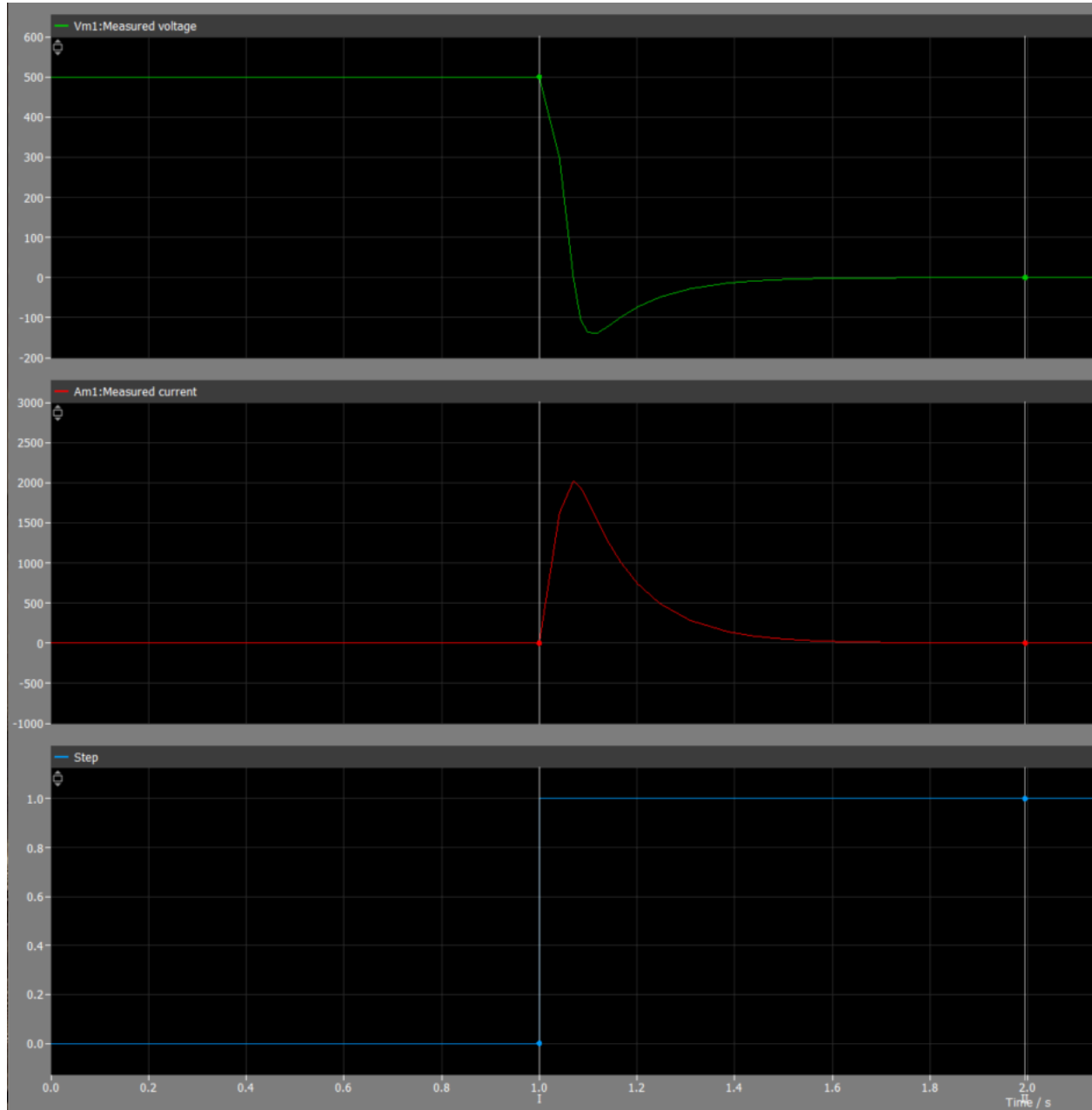

Green: Capacitor Voltage

Red: Inductor Current

Blue: My switch (activated via step function)